

Hardware Description Languages

HDLs


Hardware Description Languages




- **An HDL:**
 - Describes circuits and systems in textual format like a software program
 - It is NOT sequential like software programs
 - Can be processed by computers
 - Examples: VHDL, Verilog, AHDL, MODAL
- **Applications:** (karbord ha)
 - Simulation
 - Synthesis

Simulation and Synthesis

- **Simulation**

- Input waveform and circuit description --> 
Output waveform
ghabl az sakhte shodan
- Predicts circuit behavior before fabrication
(debug before physical implementation)

baraye narm afzar :

 


Simulation and Synthesis

- **Synthesis**

 - Automated circuit generation
- Software program takes design description and tries to find the equivalent circuit




baraye sakht afzar :




Verilog HDL

- Verilog or VHDL?
 - Similar concepts and capabilities
 - Different syntax
- Verilog:
 - Similar to C/C++ syntax
 - Case sensitive
 - Comments: //
 - ; at the end of each statement

Example

- **module:** 
 - A hardware component
 - **ports:** 
 - A component's input(s) and output(s)
 - must specify input or output or inout
 - **wires:** 
 - Intermediate signals
- inout = tarkibe input va output

```
//HDL Example 3-1
//-----
module smpl_circuit(A,B,C,x,y);
    input A,B,C;           dar parantez
                           port ha ro mizarim .
    output x,y;
    wire e;
    and g1(e,A,B);          
    not g2(y, C);
    or  g3(x,e,y);
endmodule
```

 


Fig. 3-37 Circuit to Demonstrate HDL

- **Concurrent Execution**
 - Order not important

Delays



- **Timescale:**

tik timescale

degahat

- ``timescale (time unit)/(precision)`

- **Example:** ``timescale 1ns/100ps`

yani daram migam vahede man 1ns va degahate man 0.1 ns ast .

- **1ns:** time unit
- **100ps:** precision (unit used for rounding)
- **Default:** 1ns/100ps (0.1 ns)

pas masalan age jayi time 2.345 ns dshte bashi mishe 2.3 ns .

- **Gate Delays:**

- Used by simulator to generate correct waveforms

yani delayi ke ma goftim ro shabih sazi mikone .

Delays

```
//HDL Example 3-2
//-----
//Description of circuit with delay
module circuit_with_delay (A,B,C,x,y);
  input A,B,C;
  output x,y;
  wire e; in takhir ro neshoon mide , va chon defaulte vahed ns ast .
  and # (30) g1(e,A,B); agar takhiri bayan nakoni , delay = 0 mise .
  or # (20) g3(x,e,y);
  not # (10) g2(y,C);
endmodule
```

 




Fig. 3-37 Circuit to Demonstrate HDL

Testbench

- **Testbench:** 
 - Program written to test the circuit
 - Applies the input values at the right times
 - Instantiates (calls) the module(s) 
 - Reports the outputs for evaluation

Testbench Example

Testbench:

```
//HDL Example 3-3
//-----
//Stimulus for simple circuit
module stimcrct;
  reg A,B,C;
  wire x,y;
  circuit_with_delay cwd(A,B,C,x,y);
  initial
  begin
    A = 1'b0; B = 1'b0; C = 1'b0;
    #100
    A = 1'b1; B = 1'b1; C = 1'b1;
    #100 $finish;
  end
endmodule

//Description of circuit with delay
module circuit_with_delay (A,B,C,x,y);
  input A,B,C;
  output x,y;
  wire e;
  and # (30) g1(e,A,B);
  or # (20) g3(x,e,y);
  not # (10) g2(y,C);
endmodule
```

- Doesn't have ports
- Instantiates the module
- Assigns values:
 - <size>'<base><value>
 - Base: b, o, d, h.
- ABC = “000” → “111”
- 100ns delay
- Finishes at 200ns

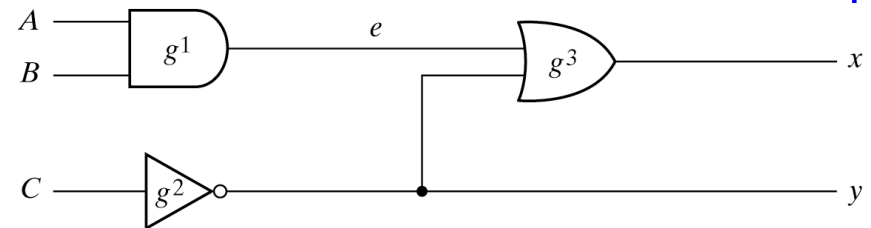


Fig. 3-37 Circuit to Demonstrate HDL

Testbench Example


 


Fig. 3-37 Circuit to Demonstrate HDL

 

baghie in ro khodeton barresi konid hatman !



shabih saz mige man nemidonam khoraji ghable 10 ns cheghadre . chon takhire not 10 ns e .

Fig. 3-38 Simulation Output of HDL Example 3-3

Primitives

- **Built-in Primitives:**
 - and, or, not, nand, nor, xor, xnor, buf
- **User-Defined Primitives (UDP):**
 - User can define by truth table
 - Use **primitive** keyword (instead of **module**)
 - Only one output but many inputs
 - first output, then inputs
 - Inputs' order must correspond with the truth table
 - Truth table between **table** and **end table**

UDP

```
//HDL Example 3-5
//-----
//User defined primitive(UDP)
primitive crctp (x,A,B,C);
    output x;
    input A,B,C;
//Truth table for x(A,B,C) = Minterms (0,2,4,6,7)
    table
//      A    B    C    :    x    (Note that this is only a comment)
      0    0    0    :    1;
      0    0    1    :    0;
      0    1    0    :    1;
      0    1    1    :    0;
      1    0    0    :    1;
      1    0    1    :    0;
      1    1    0    :    1;
      1    1    1    :    1;
    endtable
endprimitive
```

Simulation

- **ModelSim:**
 - An industrial and widely-used simulator
 - Around \$25K