

Verilog



4-Value Logic

- **Four values:**

➤ 0, 1, x, z 

- x: unknown value
- This x does NOT mean “don’t care”
- z: high impedance

input	not
0	1
1	0
x	x
z	x



and	0	1	x	z
0	0	0	0	0
1	0	1	x	x
x	0	x	x	x
z	0	x	x	x

or	0	1	x	z
0	0	1	x	x
1	1	1	1	1
x	x	1	x	x
z	x	1	x	x

Vectors

output [0:3] D;   

wire [7:0] SUM; 


➤ indexing:

– D[3]

➤ slicing:

– SUM[5:2]

Decoder

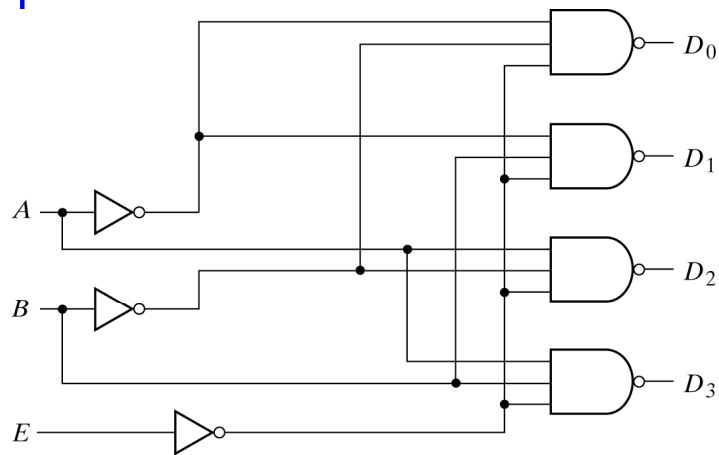


(a) Logic diagram

Fig. 4-19 2-to-4-Line Decoder with En


```
//HDL Example 4-1
//-----
//Gate-level description of a 2-to-4-line decoder
//Figure 4-19
module decoder_g1 (A,B,E,D);
    input A,B,E;
    output [0:3] D;
    wire Anot,Bnot,Enot;
    not
        n1 (Anot,A),
        n2 (Bnot,B),
        n3 (Enot,E);
    nand
        n4 (D[0],Anot,Bnot,Enot),
        n5 (D[1],Anot,B,Enot),
        n6 (D[2],A,Bnot,Enot),
        n7 (D[3],A,B,Enot);
endmodule
```

- Gate-level description
- NANDs and NOTs are instantiated in a group


Tri-State Buffers and Inverters

 


bufif1

 

bufif0

 

notif1

 

notif0

Fig. 4-31 Three-State Gates

gateName (output, input, control);

```
bufif1 (OUT, A, control);  
notif0 (Y, B, enable);
```

Multiplexer at Gate Level


- **tri:**



- A net which has the capability of being driven by more than one driver

- **Types of nets:**

 - wire, tri, supply1, supply0, wand (wired AND), wor (wired OR)
- Example:



(a) 2-to-1- line mux

mux ba estefade az tri buffer:

```
module muxtri (A, B, select, OUT);  
    input A, B, select;  
    output OUT;  
    tri OUT;  
    bufif0 (OUT, A, select);  
    bufif1 (OUT, B, select);  
endmodule;
```